

RIPPLE CARRY ADDER (64-bit)

COMPUTER-AIDED DIGITAL DESIGN

 

 







The "ripple" part comes from the fact that the carry ripples through each bit from right to left, just like ripples


N-bit Ripple Carry Adder

A Ripple carry adder is a set of simple binary adders lined up in a row.

The carry-out from each bit's addition passes to the carry-in of the next bit

 
Slow for large binary numbers because each bit's addition depends on the previous one.





1-BIT FULL ADDER


| Input | | | Output | | | |
|-------|---|-----|--------|-------|--|--|
| Α | В | Cin | Sum | Carry | | |
| 0 | 0 | 0 | 0 | 0 | | |
| 0 | 0 | 1 | 1 | 0 | | |
| 0 | 1 | 0 | 1 | 0 | | |
| 0 | 1 | 1 | 0 | 1 | | |
| 1 | 0 | 0 | 1 | 0 | | |
| 1 | 0 | 1 | 0 | 1 | | |
| 1 | 1 | 0 | 0 | 1 | | |
| 1 | 1 | 1 | 1 | 1 | | |

 


Sum = x'y'z+x'yz+xy'z'+xyzCarry = xy+xz+yz

RTL VIEW cout~1 cout~3 cout~2 sum sum


1-BIT FULL ADDER system verilog HDL

 


 


```
⊟module FA_16(
  2
               input logic [15:0] a, b,
               input logic cin,
  3
              output logic [15:0] sum,
  4
  5
              output logic cout);
  6
              wire [14:0]c;
  8
             full_adder Fa0 (a[0],b[0],cin,sum[0],c[0]);
full_adder Fa1 (a[1],b[1],c[0],sum[1],c[1]);
full_adder Fa2 (a[2],b[2],c[1],sum[2],c[2]);
full_adder Fa3 (a[3],b[3],c[2],sum[3],c[3]);
full_adder Fa4 (a[4],b[4],c[3],sum[4],c[4]);
full_adder Fa5 (a[5],b[5],c[5],sum[5],c[5]);
  9
10
11
12
13
              full_adder Fa5 (a[5],b[5],c[4],sum[5],c
14
15
              full_adder Fa6 (a[6],b[6],c[5],sum[6],c[6]);
16
              full_adder Fa7 (a[7],b[7],c[6],sum[7],c
17
              full_adder Fa8 (a[8],b[8],c[7],sum[8],c[8]);
              full_adder Fa9 (a[9],b[9],c[8],sum[9],c[9]);
full_adder Fa10 (a[10],b[10],c[9],sum[10],c[10]);
18
19
             full_adder Fa11 (a[11],b[11],c[10],sum[11],c[11]);
full_adder Fa12 (a[12],b[12],c[11],sum[12],c[12]);
full_adder Fa13 (a[13],b[13],c[12],sum[13],c[13]);
full_adder Fa14 (a[14],b[14],c[13],sum[14],c[14]);
full_adder Fa15 (a[15],b[15],c[14],sum[15],cout);
20
21
22
23
24
25
26
          endmodule
27
```

16-BIT FULL ADDER system verilog HDL

 

 

 


```
module RCA64_tb;
logic [63:0] sum;//output
logic cout;//output
logic [63:0] a,b;//input
logic cin;//input
       ⊟RCA_64 T1(
         .a(a),
.b(b),
10
         .cin(cin),
11
         .sum(sum),
12
         .cout(cout));
13
14
       ⊟initial begin
15
        a=0; b=0; cin=0;
#10 a=64'd998; b=64'd128; cin=64'd0;
#100 a=64'd9998; b=64'd9028; cin=64'd0;
16
18
19
         #50;
20
21
       Lend
22
         endmodule
23
```

TESTBENCH

a=64'd998 b=64'd128

a=64'd9998 b=64'd9028

SIMULATION

 


ADDITION OF TWO DECIMAL NUMBERS a=64'd998; b=64'd128; a=64'd998; b=64'd9028;


SUM=1126 Cout=0

SUM=25094 Cout=0



| Node Name | Direction | Location | I/O Bank | VREF Group | I/O Standard | ırrent Streng | Slew Rate |
|---------------------|-----------|----------|----------|------------|--------------|---------------|-------------|
| <u>□</u> a[3] | Input | PIN_C12 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| <mark>-</mark> a[2] | Input | PIN_D12 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| <mark>-</mark> a[1] | Input | PIN_C11 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| <mark>-</mark> a[0] | Input | PIN_C10 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| <u>⊩</u> b[3] | Input | PIN_A14 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| □ b[2] | Input | PIN_A13 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| - b[1] | Input | PIN_B12 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| ⊩ b[0] | Input | PIN_A12 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| - cin | Input | PIN_B14 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | |
| cout cout | Output | PIN_D13 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | 2 (default) |
| ° sum[3] | Output | PIN_B10 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | 2 (default) |
| sum[2] | Output | PIN_A10 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | 2 (default) |
| sum[1] | Output | PIN_A9 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | 2 (default) |
| sum[0] | Output | PIN_A8 | 7 | B7_N0 | 2.5 Vfault) | 12mAault) | 2 (default) |

 

 

THANK YOU

S.KAUSHIK

